


112-1 SoC Design Laboratory

Lab3

112061573 王語卉

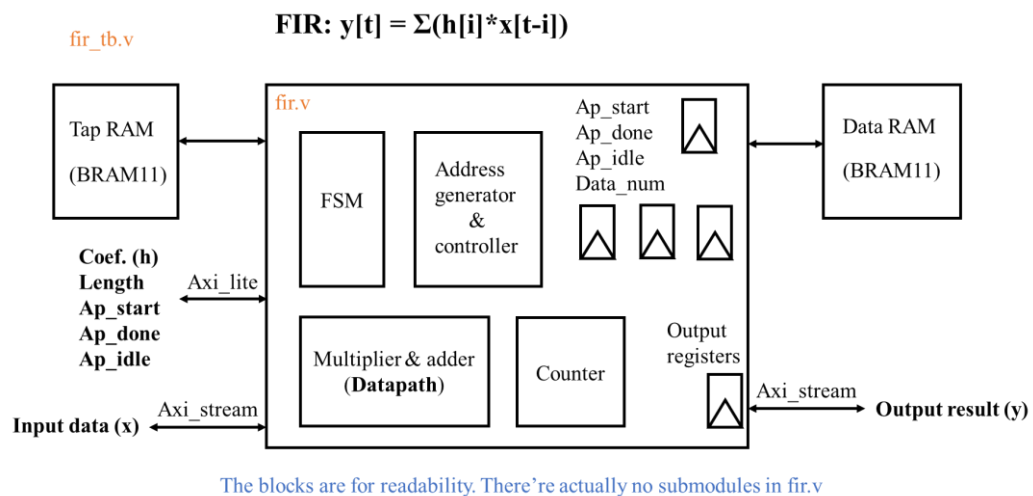
I. Block diagram

In this lab, we're going to use Verilog code to implement the FIR system. The following is the block diagram of the whole FIR system:




The input and output port have been defined. I use **bram11** for tap RAM and data RAM. There're an FSM, a multiplier and an adder, address generator and some registers in my design.

- The FSM:

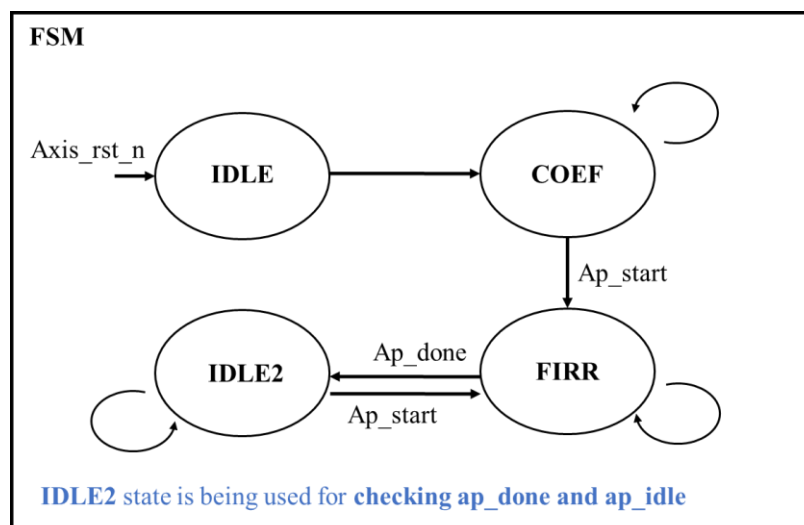

I use four states in the FSM. The **COEF** state is used for the tap RAM to store the coefficient and to read out the coefficient. The **FIRR** state is used to read data in, to store data, to read the data and coefficient out and to perform multiply and add operation. The **IDLE2** state is used to check the ap_done and ap_idle.

- The datapath and the control counter:

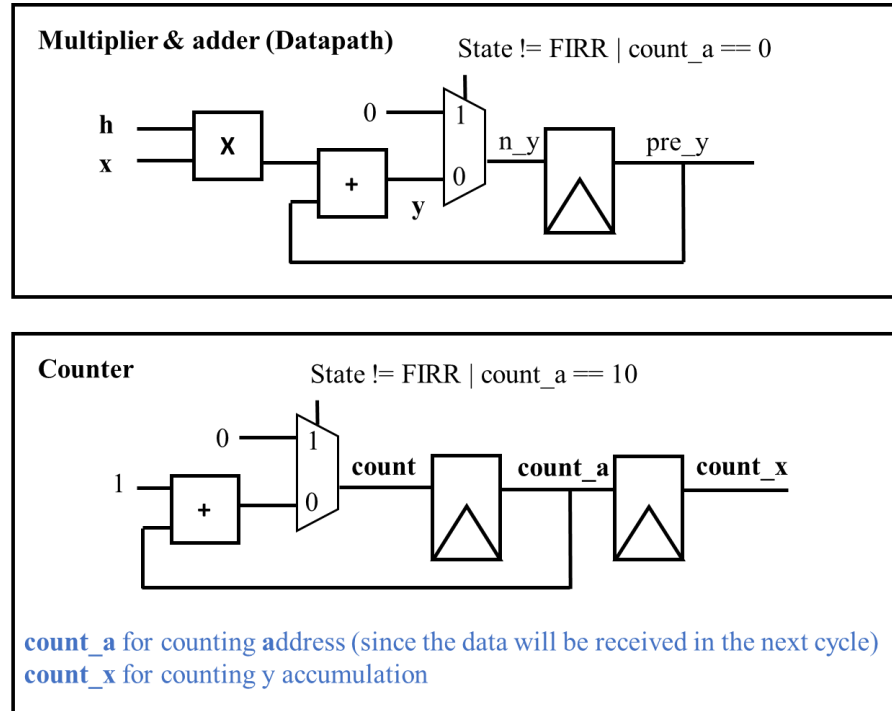


state	COEF	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR
count	0	1	2	3	4	5	6	7	8	9	10	0	1	2	3	4
count_a	0	0	1	2	3	4	5	6	7	8	9	10	0	1	2	3
count_x	0	0	0	1	2	3	4	5	6	7	8	9	10	0	1	2
y	X	X	d0	d0~d1	d0~d2	d0~d3	d0~d4	d0~d5	d0~d6	d0~d7	d0~d8	d0~d9	d0~d10	d0	d0~d1	d0~d2
n_y	0	0	d0	d0~d1	d0~d2	d0~d3	d0~d4	d0~d5	d0~d6	d0~d7	d0~d8	d0~d9	0	d0	d0~d1	d0~d2
pre_y	X	0	0	d0	d0~d1	d0~d2	d0~d3	d0~d4	d0~d5	d0~d6	d0~d7	d0~d8	d0~d9	0	d0	d0~d1


I use **count**, **count_a** (for counting RAM address) and **count_x** (for counting accumulations) to control the datapath, the address and the output control.

$\text{out_sm_tvalid} = \text{count_x} == 10$
 $\text{out_sm_tlast} = (\text{last_flag} == 1) \ \& \ (\text{count_x} == 10)$
 $\text{out_sm_tdata} = y$
 $\text{out_ss_tready} = \text{count} == 10 \ \text{//load next data}$

 (The output port are all blocked by the register, therefore the actual output will delay one cycle)




- The registers:

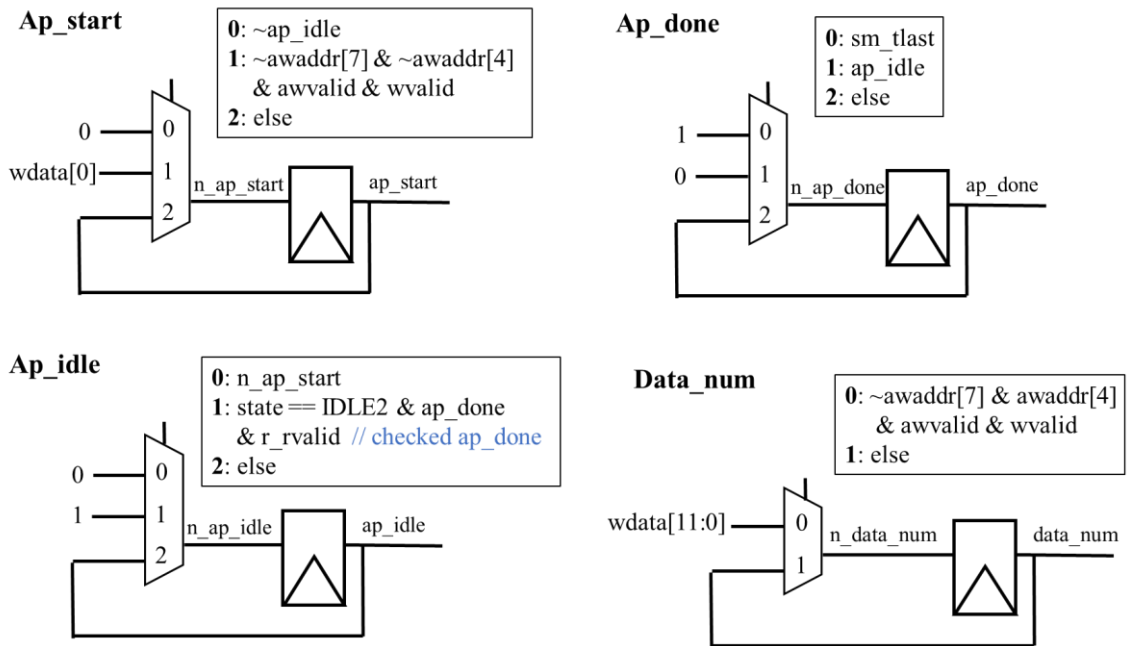

The registers are used to store the engine's current situation. Ap_done will last until ap_idle become 1. Ap_idle will become 1 after sending the ap_done signal out.

- The control signals:

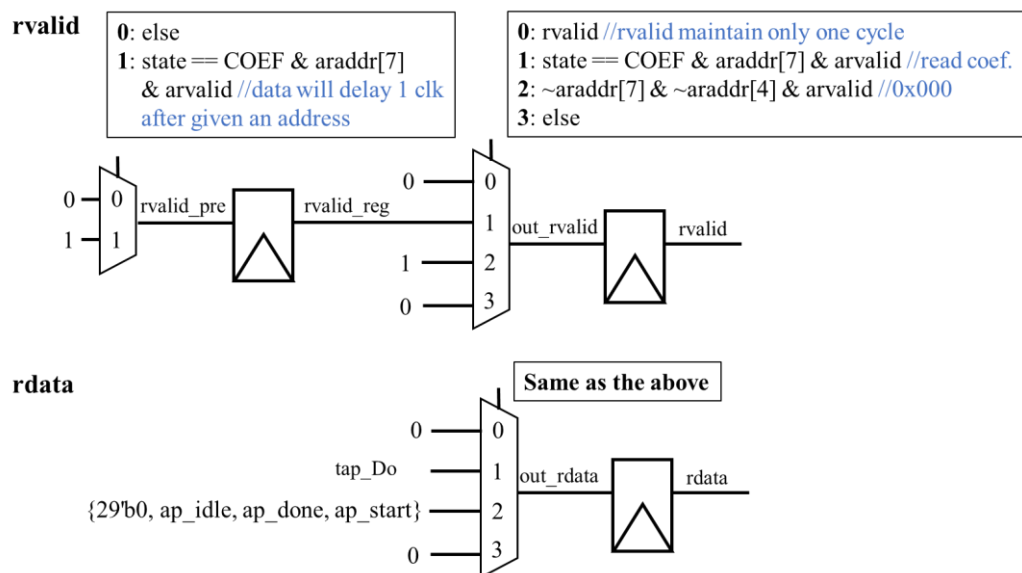

Arready = 1

Awready = wready = 1

Since the bram will output the data in the next cycle after given an address, I use one register to delay rvalid signal. Except for the COEF state that rvalid and rdata are being used to send the coefficient, they're sending ap_start/ap_done/ap_idle in other time.

The tap RAM and data RAM operations will be described in the next section.

II. Operations

The overall flow of the FIR engine is like below:

Control	State	Flow	Detail operations
	IDLE	none	
	COEF	Step1. Write	Write coefficient into tap RAM Write 0 into data RAM
		Step2. Read	Read coefficient from tap RAM
ap_start	FIRR	Every cycle	Read coefficient from tap RAM Read data from data RAM
		Every 11 cycle	Load new data x Write new data into data RAM Send the result y to the output port Update the address flag
ap_done	IDLE2	Step1. send ap_done	
		Step2. send ap_idle	

In COEF:

- In COEF state, **tap RAM** have two conditions: (1) awvalid & waddr[7] (write) (2) arvalid & raddr[7] (read).

I use **waddr[6:0]** and **raddr[6:0]** for the tap RAM address in (1) and (2) respectively.

In (1), the tap_EN and tap_WE are **wready** which means the data exchange (wready & wvalid). In (2), tap_EN is **out_rvalid** which means the output data is prepared.

- Since the **data RAM** is not initialized, I use the same address, EN and WE as tap RAM to initialize data RAM in this state.

In FIR:

- We always need to access the RAM to get the coefficient and the data. Therefore, both of the EN are always on. The address of the **tap RAM** is the **count_a**. The WE of the tap RAM is 0.
- In FIR system, the data order changes every 11 cycles. Therefore, I use an additional register as **address_flag** to store the starting address of the data RAM for every 11 cycles.
- The newest data will store in the address that “**address_flag – 1**” points to. The table represents the change of the flag and the **red word** means the newest data.

flag	1	2	3	4	5	6	7	8	9	10	0	1	2	3	4	5
cycle	0~10	11~21	22~32	33~43	44~54	55~65	66~76	77~87	88~98	99~109	110~120	121~131	132~142	143~153	154~164	165~175
address	x(data)															
0	D0	D0	D0	D0	D0	D0	D0	D0	D0	D0	D0	D11	D11	D11	D11	D11
1	0	D1	D1	D1	D1	D1	D1	D1	D1	D1	D1	D1	D12	D12	D12	D12
2	0	0	D2	D2	D2	D2	D2	D2	D2	D2	D2	D2	D2	D13	D13	D13
3	0	0	0	D3	D3	D3	D3	D3	D3	D3	D3	D3	D3	D3	D14	D14
4	0	0	0	0	D4	D4	D4	D4	D4	D4	D4	D4	D4	D4	D4	D15
5	0	0	0	0	0	D5	D5	D5	D5	D5	D5	D5	D5	D5	D5	D5
6	0	0	0	0	0	0	D6	D6	D6	D6	D6	D6	D6	D6	D6	D6
7	0	0	0	0	0	0	0	D7	D7	D7	D7	D7	D7	D7	D7	D7
8	0	0	0	0	0	0	0	0	D8	D8	D8	D8	D8	D8	D8	D8
9	0	0	0	0	0	0	0	0	0	D9	D9	D9	D9	D9	D9	D9
10	0	0	0	0	0	0	0	0	0	0	D10	D10	D10	D10	D10	D10

- The data order in every 11 cycles is represented in the next table. I use **count_a** to calculate the address.

Count_a

flag	1	2	3	4	5	6	7	8	9	10	0	1	2	3	4	5
cycle	0~10	11~21	22~32	33~43	44~54	55~65	66~76	77~87	88~98	99~109	110~120	121~131	132~142	143~153	154~164	165~175
address	x(data)															
0	D0 10	D0 9	D0 8	D0 7	D0 6	D0 5	D0 4	D0 3	D0	D0	D0	D11	D11	D11	D11	D11
1	0 0	D1 10	D1 9	D1 8	D1 7	D1 6	D1 5	D1 4	D1	D1	D1	D1	D12	D12	D12	D12
2	1 0	0 0	D2 10	D2 9	D2 8	D2 7	D2 6	D2 5	D2	D2	D2	D2	D2	D13	D13	D13
3	2 0	1 0	0 0	D3 10	D3 9	D3 8	D3 7	D3 6	D3	D3	D3	D3	D3	D3	D14	D14
4	3 0	2 0	1 0	0 0	D4 10	D4 9	D4 8	D4 7	D4	D4	D4	D4	D4	D4	D4	D15
5	4 0	3 0	2 0	1 0	0 0	D5 10	D5 9	D5 8	D5	D5	D5	D5	D5	D5	D5	D5
6	5 0	4 0	3 0	2 0	1 0	0 0	D6 10	D6 9	D6	D6	D6	D6	D6	D6	D6	D6
7	6 0	5 0	4 0	3 0	2 0	1 0	0 0	D7 10	D7	D7	D7	D7	D7	D7	D7	D7
8	7 0	6 0	5 0	4 0	3 0	2 0	1 0	0 0	D8	D8	D8	D8	D8	D8	D8	D8
9	8 0	7 0	6 0	5 0	4 0	3 0	2 0	1 0	0	D9	D9	D9	D9	D9	D9	D9
10	9 0	8 0	7 0	6 0	5 0	4 0	3 0	2 0	0	0	D10	D10	D10	D10	D10	D10

If “**count_a + flag <= 10**”, then address is “**count_a + flag**”.

If “**count_a + flag > 10**”, then address is “**count_a + flag – 11**”.

- When the address comes to “**address_flag – 1**”, i.e., the last address in every 11 cycles, I set **ss_tready** to 1 to receive the new data. At the same time, **data_WE** is also set to 1 to write the new data into data RAM. Therefore, the new data will be read out in the next cycle to perform the last accumulation in these 11 cycles. Moreover, since the next cycle will start the new 11 cycles,

the **address_flag**, i.e., the starting address, will be updated in this cycle, too.

state	COEF	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR	FIRR
count	0	1	2	3	4	5	6	7	8	9	10	0	1	2	3	4
count_a	0	0	1	2	3	4	5	6	7	8	9	10	0	1	2	3
count_x	0	0	0	1	2	3	4	5	6	7	8	9	10	0	1	2
y	X	X	d0	d0~d1	d0~d2	d0~d3	d0~d4	d0~d5	d0~d6	d0~d7	d0~d8	d0~d9	d0~d10	d0	d0~d1	d0~d2
n_y	0	0	d0	d0~d1	d0~d2	d0~d3	d0~d4	d0~d5	d0~d6	d0~d7	d0~d8	d0~d9	0	d0	d0~d1	d0~d2
pre_y	X	0	0	d0	d0~d1	d0~d2	d0~d3	d0~d4	d0~d5	d0~d6	d0~d7	d0~d8	d0~d9	0	d0	d0~d1
address	X	1	2	3	4	5	6	7	8	9	10	0	2	3	4	5
flag	1	1	1	1	1	1	1	1	1	1	1	1	1	2	2	2
data_WE	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
out_ss_tready	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
ss_tready	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
													write D1 to addr 0			
													D1 is read out to calculate d10			
													Update the flag			

- If count_x == 10, then we output the result y, and out_sm_tvalid will be 1. If the last_flag is 1, out_sm_tlast will be 1. When sm_tlast become 1, then ap_done will become 1.

III. Resource usage

1. Slice Logic

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	142	0	0	53200	0.27
LUT as Logic	142	0	0	53200	0.27
LUT as Memory	0	0	0	17400	0.00
Slice Registers	122	0	0	106400	0.11
Register as Flip Flop	122	0	0	106400	0.11
Register as Latch	0	0	0	106400	0.00
F7 Muxes	0	0	0	26600	0.00
F8 Muxes	0	0	0	13300	0.00

2. Memory

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

There're no bram in my design.

IV. Timing report

Clock Summary

Clock	Waveform(ns)	Period(ns)	Frequency(MHz)
axis_clk	{0.000 7.500}	15.000	66.667

From Clock: axis_clk
To Clock: axis_clk

Setup :	0	Failing Endpoints, Worst Slack	0.477ns, Total Violation	0.000ns
Hold :	0	Failing Endpoints, Worst Slack	0.140ns, Total Violation	0.000ns
PW :	0	Failing Endpoints, Worst Slack	7.000ns, Total Violation	0.000ns

Max Delay Paths

Slack (MET) :	0.477ns (required time - arrival time)
Source:	araddr[7] (input port clocked by axis_clk {rise@0.000ns fall@7.500ns period=15.000ns})
Destination:	data_A[5] (output port clocked by axis_clk {rise@0.000ns fall@7.500ns period=15.000ns})
Path Group:	axis_clk
Path Type:	Max at Slow Process Corner
Requirement:	15.000ns (axis_clk rise@15.000ns - axis_clk rise@0.000ns)
Data Path Delay:	6.988ns (logic 3.978ns (56.932%) route 3.009ns (43.068%))
Logic Levels:	5 (IBUF=1 LUT3=1 LUT6=2 OBUF=1)
Input Delay:	3.750ns
Output Delay:	3.750ns
Clock Uncertainty:	0.035ns $((TSJ^2 + TIJ^2)^{1/2} + DJ) / 2 + PE$
Total System Jitter	(TSJ): 0.071ns
Total Input Jitter	(TIJ): 0.000ns
Discrete Jitter	(DJ): 0.000ns
Phase Error	(PE): 0.000ns

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
	(clock axis_clk rise edge)	0.000	0.000	r
	input delay	3.750	3.750	
	net (fo=0)	0.000	3.750	r araddr[7] (IN) r araddr_IBUF[7]_inst/I
	IBUF (Prop_ibuf_I_0)	0.972	4.722	r araddr_IBUF[7]_inst/O
	net (fo=34, unplaced)	0.800	5.521	r araddr_IBUF[7] r out_rvalid_reg_i_1/I2
	LUT3 (Prop_lut3_I2_0)	0.124	5.645	r out_rvalid_reg_i_1/O
	net (fo=12, unplaced)	0.497	6.142	r out_rvalid_pre r tap_A_OBUF[5]_inst_i_1/I3
	LUT6 (Prop_lut6_I3_0)	0.124	6.266	r tap_A_OBUF[5]_inst_i_1/O
	net (fo=2, unplaced)	0.913	7.179	r tap_A_OBUF[5] r data_A_OBUF[5]_inst_i_1/I0
	LUT6 (Prop_lut6_I0_0)	0.124	7.303	r data_A_OBUF[5]_inst_i_1/O
	net (fo=1, unplaced)	0.800	8.103	r data_A_OBUF[5] r data_A_OBUF[5]_inst/I
	OBUF (Prop_obuf_I_0)	2.634	10.738	r data_A_OBUF[5]_inst/O
	net (fo=0)	0.000	10.738	r data_A[5] r data_A[5] (OUT)
	(clock axis_clk rise edge)	15.000	15.000	r
	clock pessimism	0.000	15.000	
	clock uncertainty	-0.035	14.965	
	output delay	-3.750	11.215	
	required time		11.215	
	arrival time		-10.738	
	slack		0.477	

V. Simulation waveform

